

EE 105 Spring 2026

Prelab Worksheet 1: Electronic Test Equipment, RC response, diode IV

Name(s): _____

Lab Section: _____

Submit this worksheet to Gradescope before your lab section the week it is due.

1

$V_{out} =$ _____ $I_{20k} =$ _____

2.1

Time Constant, $\tau =$ _____

2.2

Transfer Function, $H(s) =$ _____

2.3

Pole frequency: $\omega_p =$ _____ , $f_p =$ _____

2.4

Bode Plot:

2.5

Formula for C, given magnitude: $C = \underline{\hspace{10cm}}$

2.6

Formula for C, given phase: $C = \underline{\hspace{10cm}}$

3.1

Time Constant, $\tau = \underline{\hspace{10cm}}$

3.2

Transfer Function, $H(s) = \underline{\hspace{10cm}}$

3.3

Pole frequency: $\omega_p = \underline{\hspace{10cm}}$, $f_p = \underline{\hspace{10cm}}$

3.4

Bode Plot:

4.1

If $V_{out} = 0$ V, I = _____

4.2

If $V_{out} = 1$ V, I = _____

4.3

IV Curve: